

## Computational physics

09-02-2017

In the figure, a  $RLC$  circuit is sketched. It is made of a voltage generator  $V(t)$ , a resistor  $R$ , an inductor  $L$  and a capacitor  $C$ .

The equation governing the evolution in time of the current  $I(t)$  crossing the circuit is given by:

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I(t) = \frac{V'(t)}{L}$$


where:  $V'(t)$  is the time derivative of the applied voltage.

The student should solve the above equation with a second order Runge-Kutta time scheme for a constant input voltage  $V(t) = V_0$  and several combinations of parameters  $R$ ,  $L$  and  $C$  in the following regimes:

$$\frac{R}{2} \sqrt{\frac{C}{L}} < 1 \quad \text{underdamped regime;}$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} > 1 \quad \text{overdamped regime;}$$
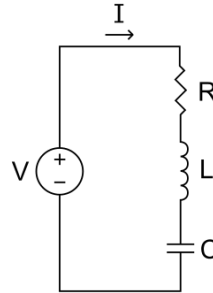
$$\frac{R}{2} \sqrt{\frac{C}{L}} = 1 \quad \text{critically damped regime.}$$



with initial conditions:  $I(t = 0) = 0$  and  $I'(t = 0) = 1$ , by discussing how the solution changes in the three regimes.

Then, by fixing three values at choice for  $R$ ,  $L$  and  $C$  and by using a sinusoidal input voltage  $V(t) = V_0 \sin(\omega t)$  show that, for at least 7 different values of  $\omega$ , the amplitude of the output current  $I$  has a maximum for a frequency:  $\omega_0 = 1/\sqrt{LC}$ .

In this case, use the initial conditions:  $I(t = 0) = 0$ ,  $I'(t = 0) = V_0 \omega / R$ .